
EE 2010
Fall 2026


Name _____


Game 28
10/7/2026

Note: The two op-amps in this game are not the standard form (due to R_2). So, you should be using node voltage to solve them

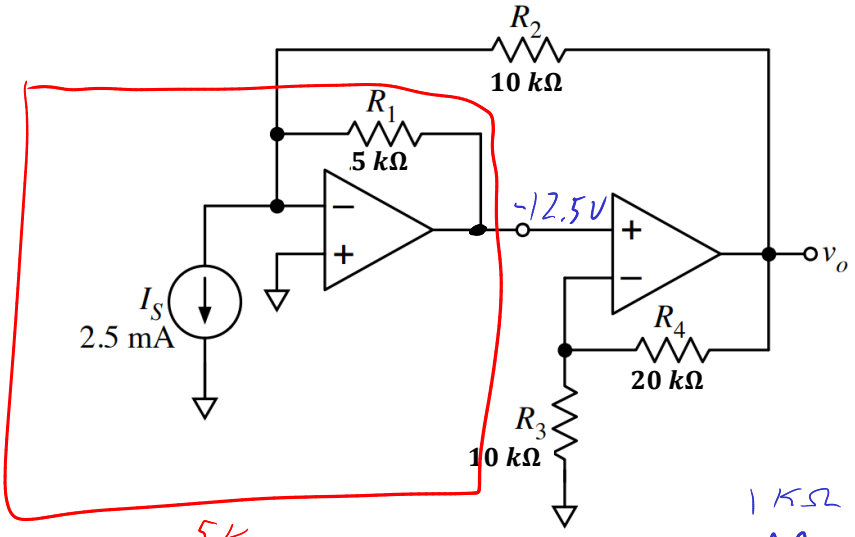a) Calculate the value of v_o in the circuit below.
b) Determine the current absorbed or generated at the output of each amplifier.



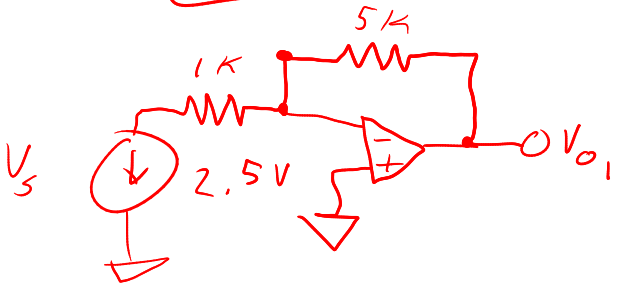

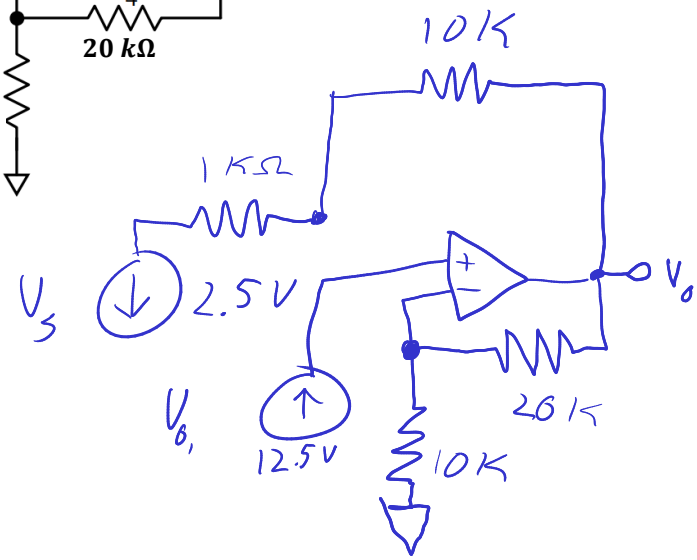

$V_{o_1} = -5V_S = -12.5V$

$\frac{V_- - 0}{10} + \frac{V_- - V_o}{20} = 0$

$3V_- = V_o \qquad V_o = 37.5V$