EE 2010
Fall 2026


Name _____

Game 3
08/25/2026

For the following circuit find the power associated with each element and answer the following questions.

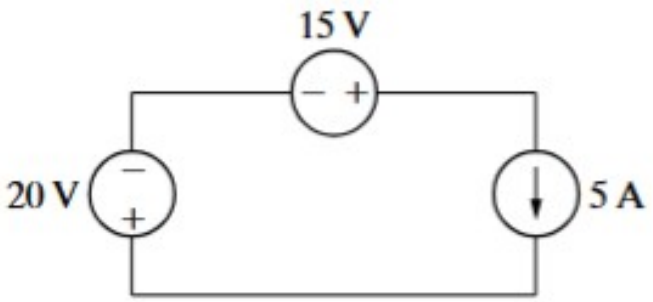a) **Which sources are generating power? Why?**
b) **Which sources are absorbing power? Why?**

Hint: First identify the direction of current.



(a) 15V & 5A generate
5A directs current from 15V
to 20V at 5A

(b) 20V absorbs
20V has 25VA flow into it