EE 2010
Fall 2026

Name Wyatt Evans

Game 30
10/9/2026

a) Find the equivalent inductance, L_{eq}, and the initial current in the equivalent inductor, i_L, for the circuit on the left
Hint: Use KCL to find i_L

b) Find the equivalent capacitance, C_{eq}, and the initial voltage across the equivalent capacitor, v_C, for the circuit on the right
Hint: Use KVL to find v_C



