
EE 2010
Fall 2026

Name Wyatt Evans


Game 4b
08/31/2026

For each circuit:

Simplify the circuit to the simplest form by reducing the resistor network and show all steps (by the end there should only be one power source and one resistor)

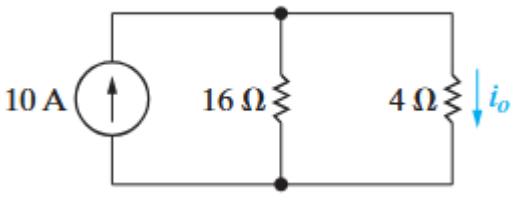

Circuit 1

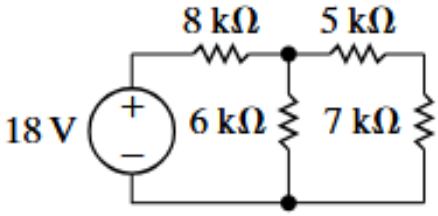

Circuit 2

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$R_{eq} = \frac{1}{\left(\frac{5}{16}\right)} = \frac{16}{5} = 3.2\,\Omega$$

